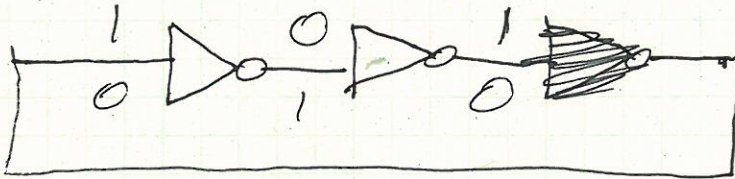



Combinational Logic - outputs depend on current inputs

Sequential Logic - outputs depends on current & prior inputs


⇒ requires memory - somewhere to store prior inputs.




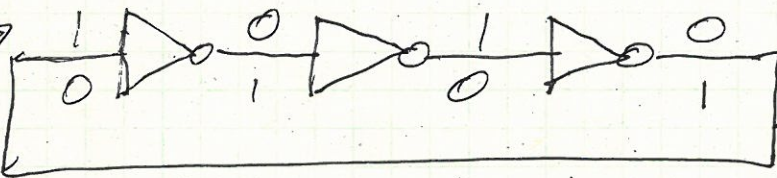
Bistable Element
Fundamental building block of memory



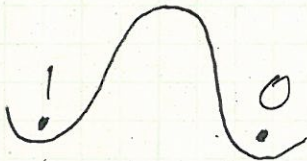Astable Element
Book calls it a ring oscillator



SR Latch: simplest sequential circuits

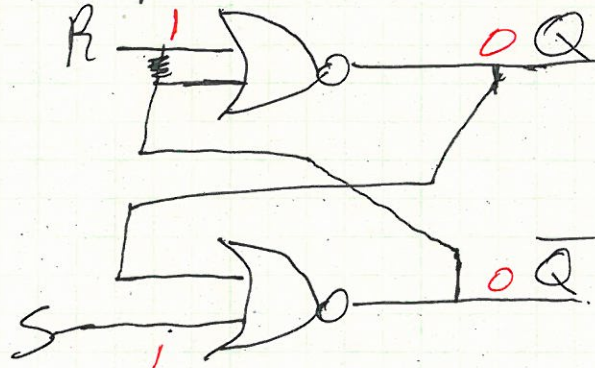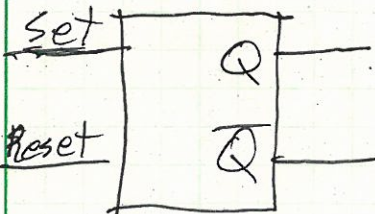


S	R	Q	Q̄
1	0	1	0
0	0	Q _{prev}	Q̄ _{prev}
0	1	0	1
0	0	Q _{prev}	Q̄ _{prev}
1	1	0	0

set state (1)


reset state (0)

undefined & we have no idea what the next state will be

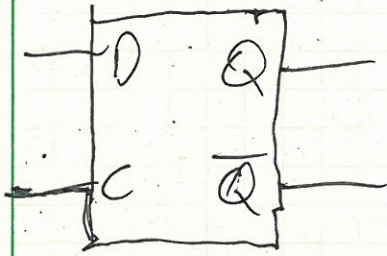D-Latch: Solves the issues of the SR-latch when S & R are both asserted



C	D	Q
0	X	Q _{prev}
1	0	0
1	1	1

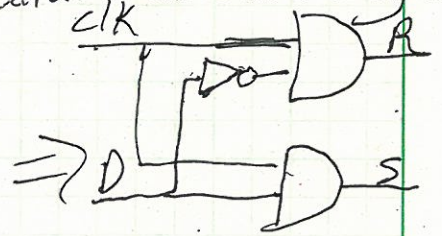

Transparent: when control is High Q will follow input

Opaque: when control is Low Q won't change




ADD D-Latch before SR

D	R	S
X	0	0
1	1	0
0	0	1

D-latch updates its state continuously while CLK is '1'

Flip Flops: Copies D to Q on rising edge of CLK & remembers it. Its state on all others

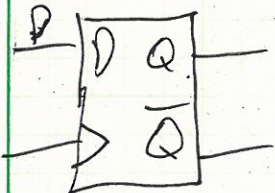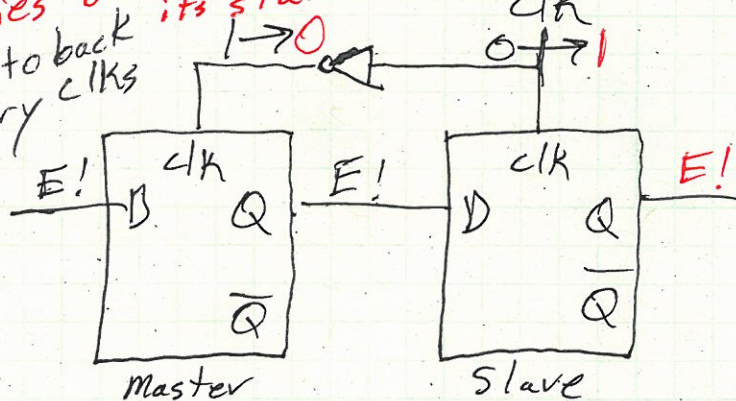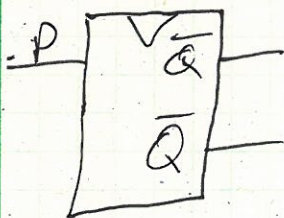D-F/F: 2 D-latches w complementary clocks



CLK	D	Q
0	0	Q _{prev}
0	1	Q _{prev}
1	0	Q _{prev}
1	1	Q _{prev}
↑	0	0
↑	1	1

rising edge

active low Reset

Negative (falling) edge triggered


if EN=1
⇒ no change to F/F

Synchronous circuit - combinational circuit followed by flip flops

Properties:

- Every circuit element is either a register or a combinational circuit
- At least one circuit is a register
- All registers have the same clock
- Every cyclic path contains at least one register

Register - An N-bit Register is a bank of N-FlipFlops


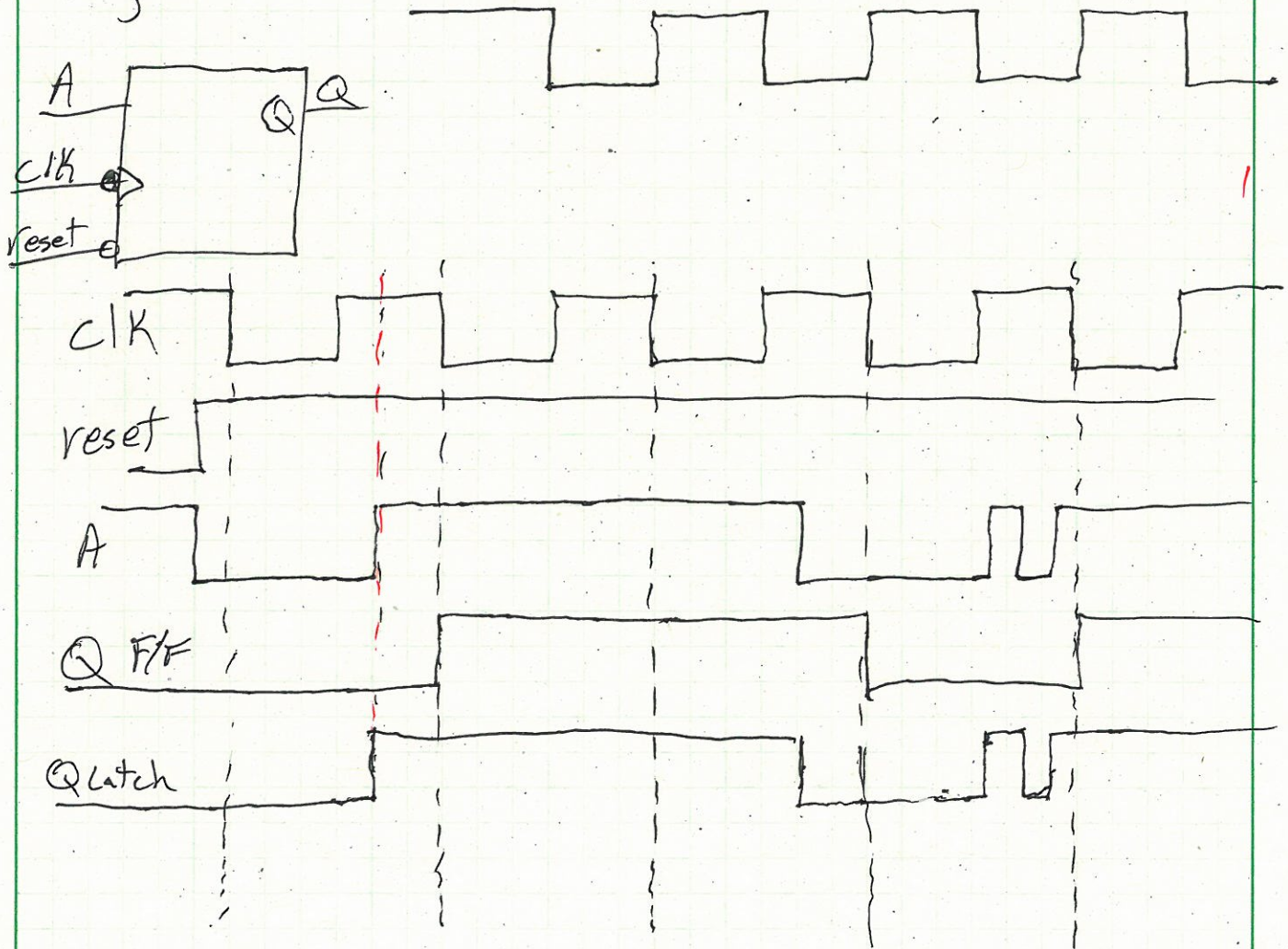


Lesson 10 – Introduction to Synchronous Circuits

Combinational logic –

Sequential logic –

SR Latch

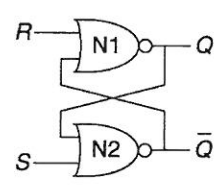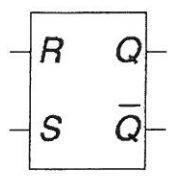


S	R	Q	Q'

S =
R =
Q =


Q changes _____

Problem with SR latch:

D Latch

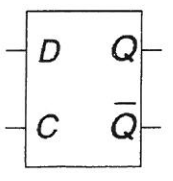

C	D	Q	Q'

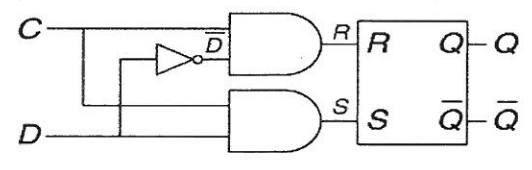

C =
D =
Q =


transparent –

opaque –

Q changes _____

Problem with D latch:

D Flip-Flop

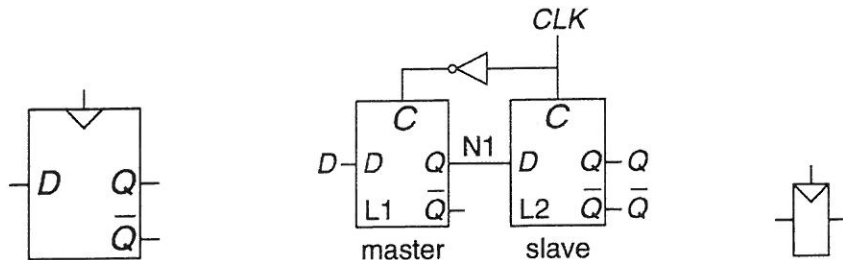

CLK	D	Q	Q'
0	0		
0	1		
1	0		
1	1		
↑	0		
↑	1		



CLK =
D =
Q =

Comprised of:

Q changes _____

Enabled flip-flop –

Resettable flip-flop –

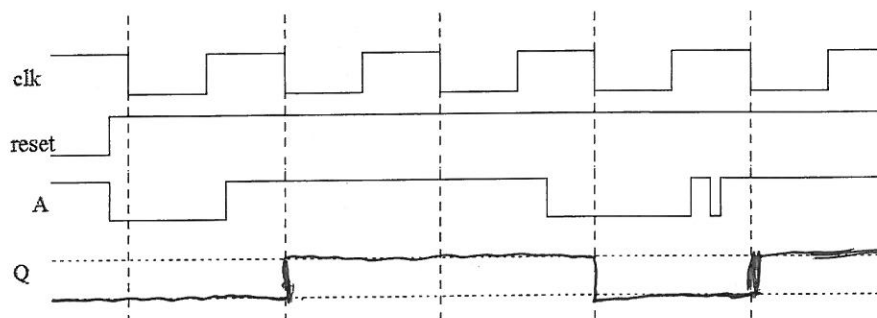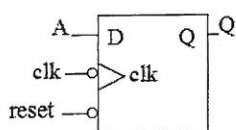

*What is the difference between a latch and a flip flop?

Register –

Synchronous circuit –

- Properties:
- a)
 - b)
 - c)
 - d)

Example:

Asynchronous circuit –