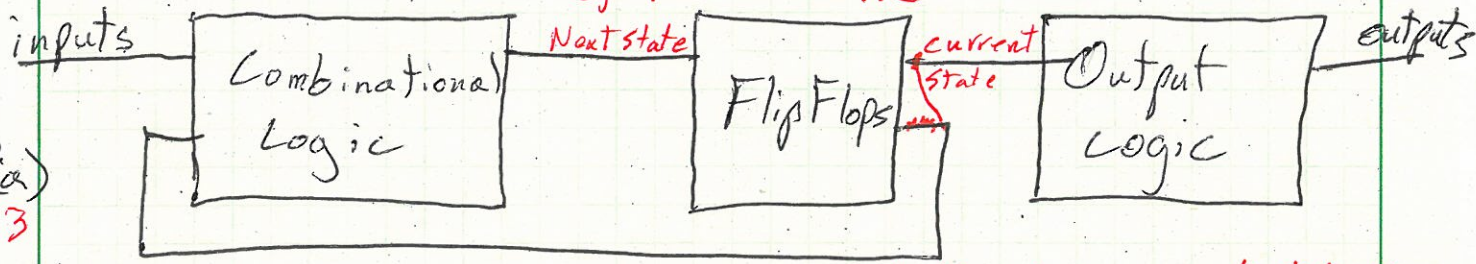



Overview:

- FSMs
- Design

HW due LSN 14

FSM - M -inputs, N -Outputs, & K -Bits of stateThey have K registersFinite State Machine (FSM): can be in one of a finite number (2^K) state-unique statesMoore Machine: ^{outputs} - only depends on the current state of the machine

see Fig 3.22(a) p. 123

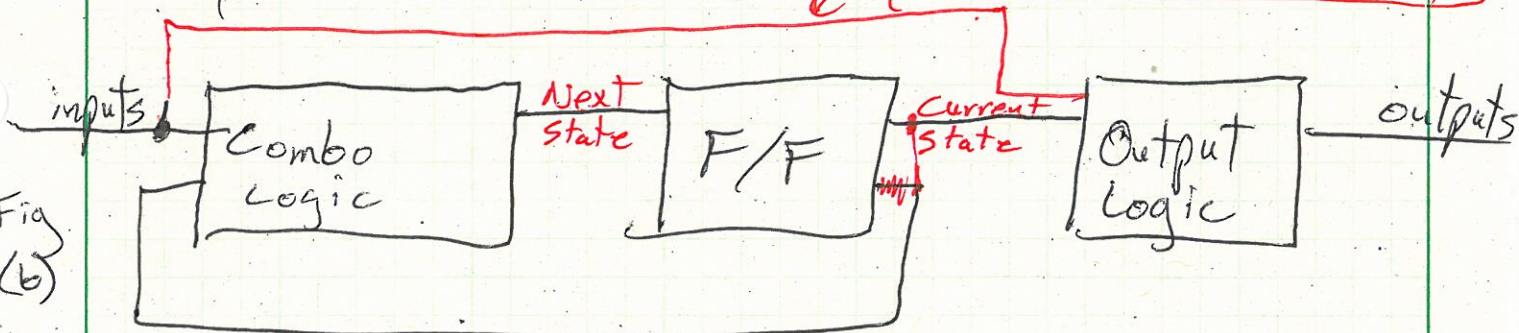Mealy Machine - outputs depend on both the current state & current inputs, only diff btwn Moore & Mealy

see Fig 3.22(b)

How to design a state machine:

- 0) Description
 - 1) state transition diagram
 - 2) state transition & output tables
 - 3) next state & output equations
 - 4) schematic

o) Vending machine


- Tea = 50¢

- No change given

- Only accepts 25¢

Inputs: C = coin
also a clock

Output: Tea

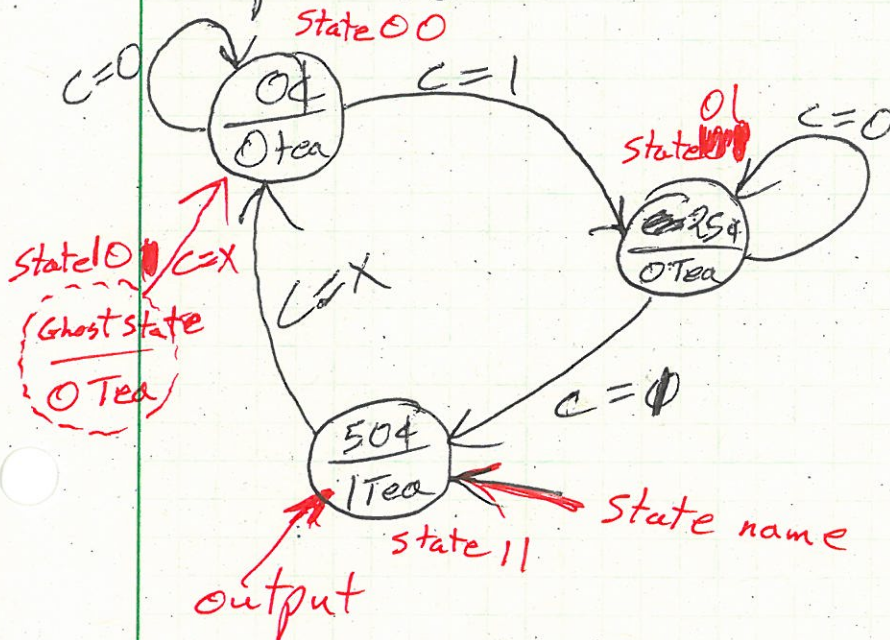

State Transition
Diagram
(moore machine)

★ Need to account for all states

- The ghost state could be ^{our} reset state
- when we turn on machine we need
to account for all possible states

State Table:

2) coin? →

Current State	A	B	C	A*	B*
000	0	0	0	0	0
001	0	0	1	0	1
010	0	1	0	0	1
011	0	1	1	1	1
100	1	0	0	0	0
101	1	0	1	0	0
110	1	1	0	0	0
111	1	1	1	0	0

Next State

Output table:


A	B	T
0	0	0
0	1	0
1	0	0
1	1	1

3) Equations

$$T = AB$$

$$A^* = \bar{A}BC$$
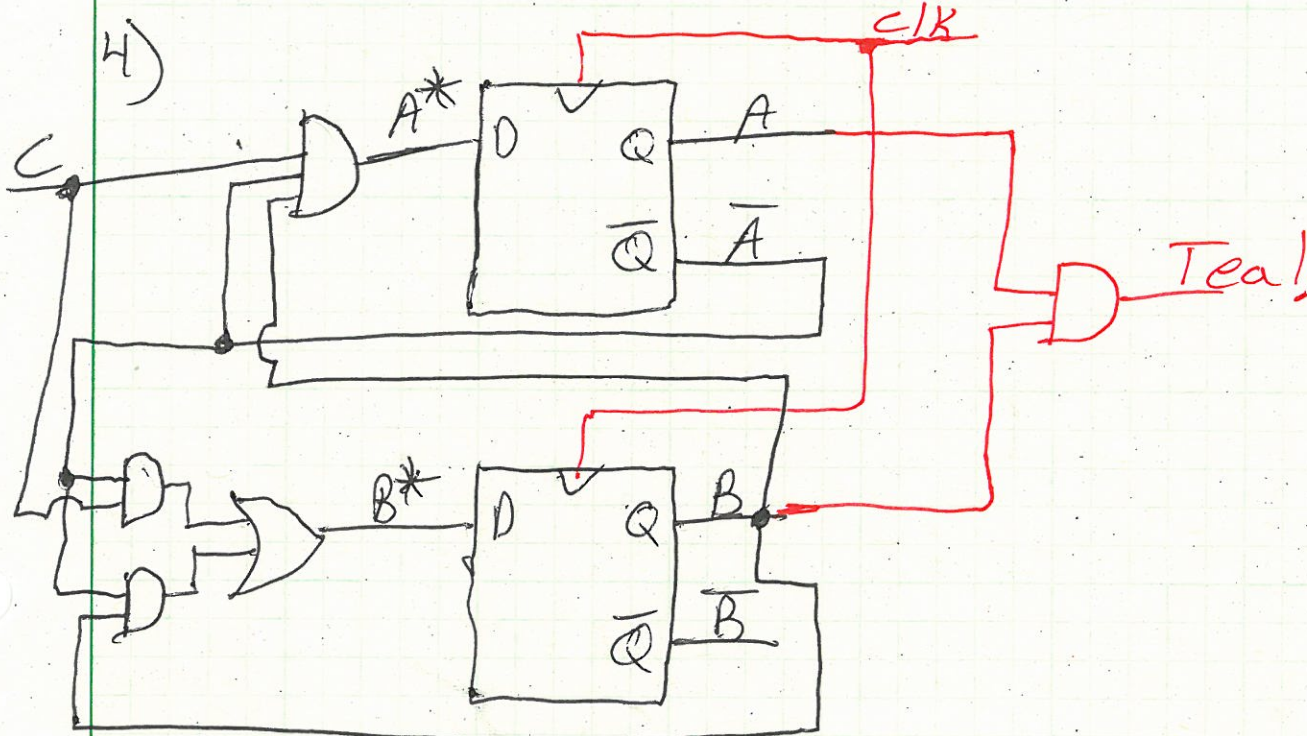
$$B^* = \bar{A}\bar{B}C + \bar{A}B = \bar{A}B + \bar{A}C$$




Real Life examples of statemachines:

- Soda machine
- Software Applications
- spell checker - using soundex
- Driving to school/work

Mealy Machine:

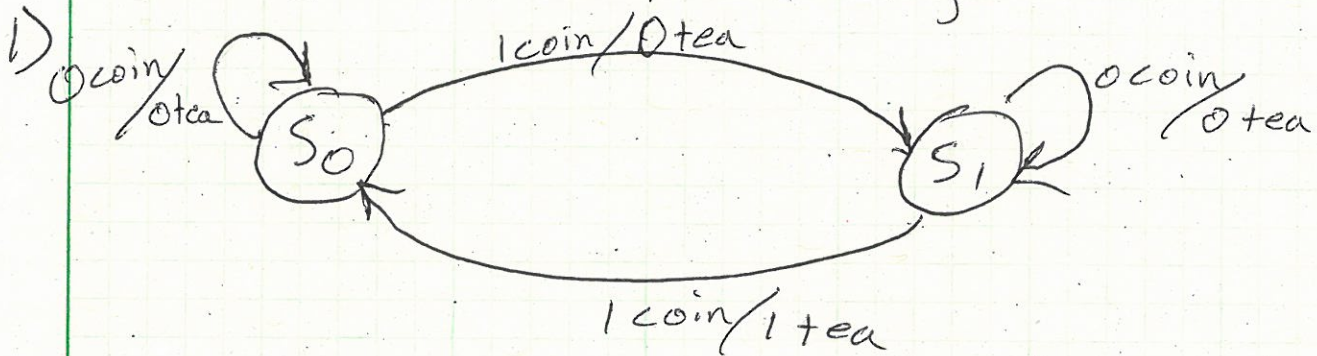- Potential for less states
- More difficult to design



- outputs tied to arcs

How many F/Fs do we need? 1

2)


State	C	State*	T
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

3)

$$T = SC$$

$$S^* = \bar{S}C + S\bar{C}$$

4)

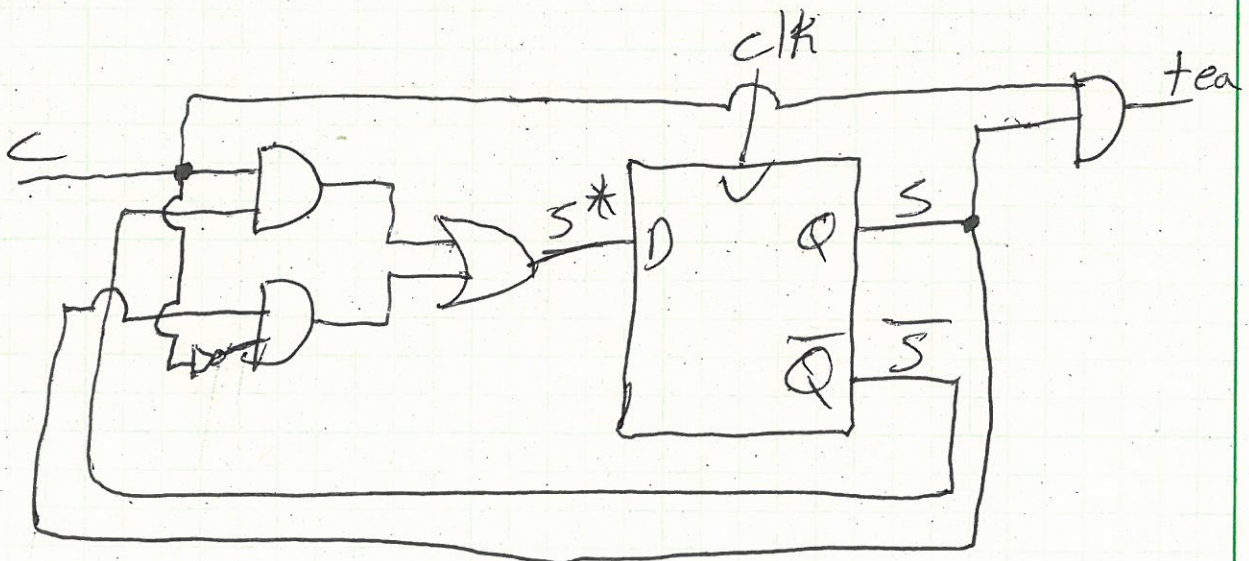

Board work:

- Draw me a picture of a mealy or moore state machine that shows
Transition Diagram
- A snail is crawling across numbers a sequence of Numbers and he smiles if the last 2 #s are "01" book Does "01" Have them use "11" makes him smile

Example 3.7 on p 132

Sequence

