
 


Overview:


- VHDL

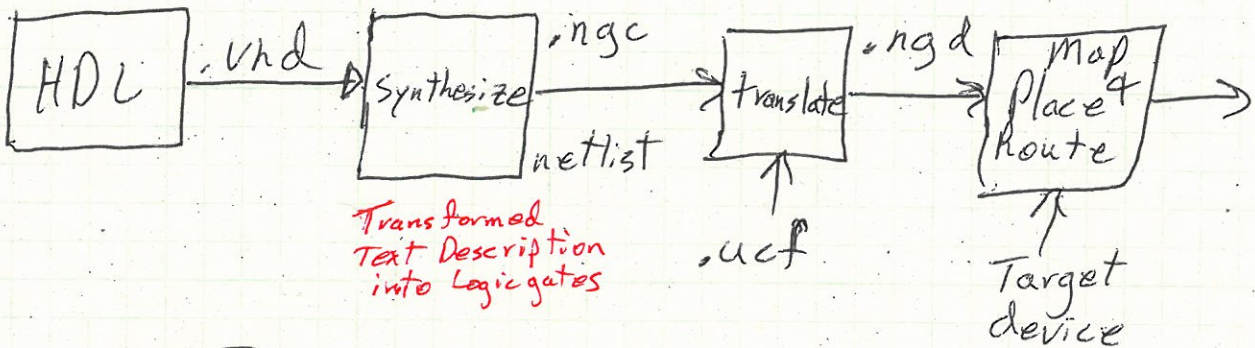VHDL - ^(VHSIC) Very High Speed Integrated Circuits Hardware Description Language




VHDL is not sequential like (C, Java, & Python)
everything happens all at once

entity - defines inputs & outputs

 

 architecture - describes what is inside the box



* Red indicates protected/reserved words!

```

entity ent_name is
    port (port_name : mode signal type);

```

In, out
 std logic
 std logic vector

```

architecture arch_name of ent_name is
    signal declarations
    component declarations
begin
    connect your stuff;
end arch_name;

```


Behavioral vs Structural:


Signal Declarations — behavioral / structural
 component declarations — structural

Behavioral — Describing a module in terms of the relationships
 between inputs & outputs
~~Structural~~ — describing a module in terms of how it is
 composed of simpler modules

Exercise: 4.5


Minority

A B C	Y
0 0 0	1
0 0 1	1
0 1 0	1
0 1 1	0
1 0 0	1
1 0 1	0
1 1 0	0
1 1 1	0

 

$$Y = \bar{A}\bar{B} + \bar{A}\bar{C} + \bar{B}\bar{C}$$

 First do an example of behavioral: implement in VHDL
 How else can we do it?
 Structural:



Create minority 2