

```
1  -----
2  -- Name: Capt Jeff Falkinburg
3  -- Date: Spring 2016
4  -- Course: ECE 281
5  -- File: Lsn20_stoplight.vhd
6  -- HW:   Lecture 20
7  -- Purp: Basic Stoplight State Machine
8  -- Doc:  None
9  -- Academic Integrity Statement: I certify that, while others may have
10 -- assisted me in brain storming, debugging and validating this program,
11 -- the program itself is my own work. I understand that submitting code
12 -- which is the work of other individuals is a violation of the honor
13 -- code. I also understand that if I knowingly give my original work to
14 -- another individual is also a violation of the honor code.
15 -----
16 library IEEE;
17 use IEEE.STD_LOGIC_1164.ALL;
18
19 entity stoplight is
20     Port ( C : in  STD_LOGIC;
21           reset : in  STD_LOGIC;
22           clk : in  STD_LOGIC;
23           R : out  STD_LOGIC;
24           Y : out  STD_LOGIC;
25           G : out  STD_LOGIC);
26 end stoplight;
27
28 architecture Behavioral of stoplight is
29
30     type stoplight_state is (red, green, yellow);
31     signal next_state, current_state : stoplight_state;
32
33     begin
34
35         --next state logic
36         process (C, current_state)
37         begin
38             case current_state is
39                 when red =>
40                     if C = '1' then
41                         next_state <= green;
42                     else
43                         next_state <= red;
44                     end if;
45                 when green =>
46                     if C = '1' then
47                         next_state <= green;
48                     else
49                         next_state <= yellow;
50                     end if;
51                 when yellow =>
52                     next_state <= red;
53                 when others =>
54                     next_state <= red;
55             end case;
56         end process;
57
```

```
58  --Alternate next state logic
59  -- next_state <=  green when (current_state = red and C = '1') else
60  --                  red when (current_state = red and C = '0') else
61  --                  green when (current_state = green and C = '1') else
62  --                  yellow when (current_state = green and C = '0') else
63  --                  red when (current_state = yellow) else
64  --                  red;
65
66  -- state memory
67
68  process (clk, reset) -- Only the state flip-flop needs to be in a process
69  begin               -- But we went through a case example for continuity
70      if reset = '1' then
71          current_state <= yellow; -- Reset into yellow
72      elsif (rising_edge(clk)) then
73          current_state <= next_state;
74      end if;
75  end process;
76
77  -- output logic
78
79  R <= '1' when current_state = red else '0';
80  G <= '1' when current_state = green else '0';
81  Y <= '1' when current_state = yellow else '0';
82
83
84  end Behavioral;
85
86
```