

Overview:

- VHDL

- sequential logic

- HW#3 Due Lesson 22

- Do midterm feedback

Entity - box w/ ports I/O

Architecture - Describes what is inside the box

- Two types of Arch description

- Behavioral

- Structural - Described

Process - "box" that listens for signals (wires)

- when signal changes, process runs

- Can be scary!

- adds memory

- harder to visualize circuit

- If you want a FlipFlop you need a process.

generic:

process (sensitivity list)

statements

end process;

specific:

process (A, B)

Y <= A and B;

end process;




not in Process:

$y \leftarrow A \text{ or } C;$

$y \leftarrow A \text{ and } B;$

$y \leftarrow \text{C and } D;$

 

If statements are not in a process, which gets assigned to y ?

-- All of them

Is this bad?

-- yes

-- gives us potential for 'X' illegal values

process (A, B, C, D)


$y \leftarrow A \text{ or } C;$

$y \leftarrow A \text{ and } B;$

$y \leftarrow C \text{ and } D;$


end process;

-- what outputs?

 

schedule is over written!!

change sensitivity list to (C, D)

 

change sensitivity list to (C)



Implicitly creates memory due to sensitivity list since it remembers what it was

Create a D-F/F in VHDL:

entity **Flop** is

port (**clk**, **D** : in std_logic;
Q : out std_logic);

end;

architecture

synth of **flop** is ^{could be named Behavioral, structural, structural, synth}
 begin ^{Build stuff (otherwise, behavior)}

process (**clk**)

if rising-edge (**clk**) then

Q <= D;

end if;

end process;

end synth;

we only want it evaluated on rising edge of clk.

only runs when clk changes

only when rising edge
 0 → 1

How do we change process to implement a D-Latch?

{ if **clk** = '1'
Q <= **D**;
 end if;

DO NOT USE:

clk'event and **clk = '1'**

Do use instead?

rising-edge (clk)

why? - we don't want to add logic gates to a clock line, but if it is a control line then it is ok.

Variables: - only exist in process.

→ assigned values based on Blocking statement

$:=$ instead of $<=$

- values assigned immediately

- No scheduling

- Blocking statement:

- evaluated in order they appear

- non Blocking statement:

- evaluated concurrently

- signals updated later

process (A, B)

variable tmp : std_logic;

begin

tmp := '0';

tmp := tmp or A;


tmp := tmp or B;

y <= tmp

end process;

What does our schematic look like?

Problem?

 

Process (AB) *eliminate variable*

begin

tmp <='0';

tmp <= tmp or A;

tmp <= tmp or B;

y <= tmp;

end process;

*poor example of
VHDL assigning
a signal multiple
times.*



Rules for Process:

1) think before using variables

2) avoid "innovative" use of language constructs

* 3) avoid overwriting a signal

* 4) Only use processes for sequential circuits

* Only for ECE 281 outside of class use sparingly

4.13 Write VHDL ^{module} for 2:4 Decoder

4.15 Write VHDL module to implement:

a) $Y = AC + \bar{A}\bar{B}C$

b) $Y = \bar{A}\bar{B} + \bar{A}B\bar{C} + \overline{(A+C)}$

Decoder 2:4

